

What signals we know?

① Sinusoidals

$$s(t) = A \cos(2\pi f_0 t + \theta)$$


② Complex Exponentials

$$s(t) = A e^{j(2\pi f_0 t + \theta)}$$

↗ Re
↘ Im

③ Real exponential

$$s(t) = A e^{-\frac{t}{\tau}}$$

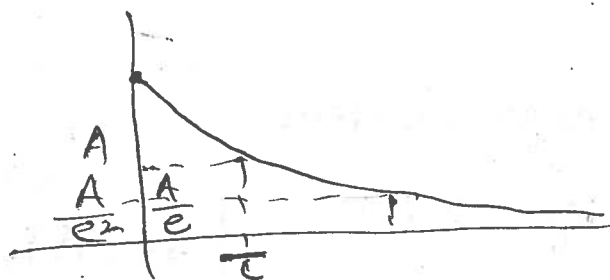

③ Unit step

④ Unit Pulse


⑤ Square Wave

Example 1: Given $x(t)$, draw $x(t-\tau)$, $x(t+\tau)$
(delay) advance


$x(2t)$, $x(t/2)$, $x(2t-1)$

Ans -


$$x(t) =$$

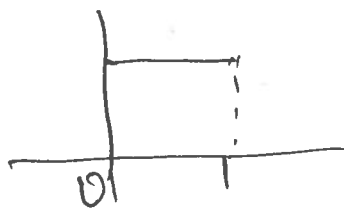


$$x(t-\tau) =$$

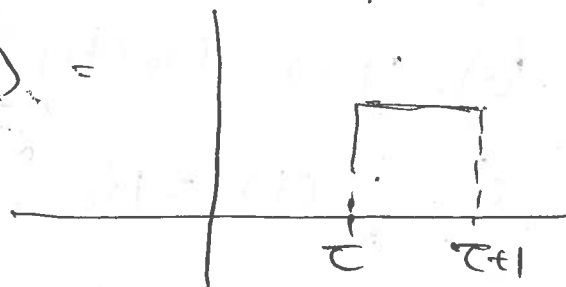


$$x(t+\tau) =$$

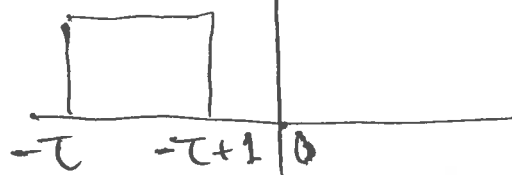


$$x(2t) =$$

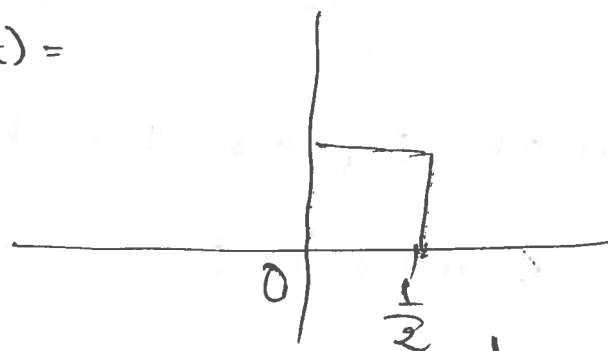

$$x(t/2) =$$


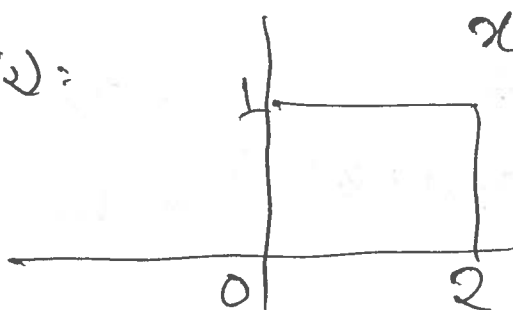


$$x(2t-1) =$$

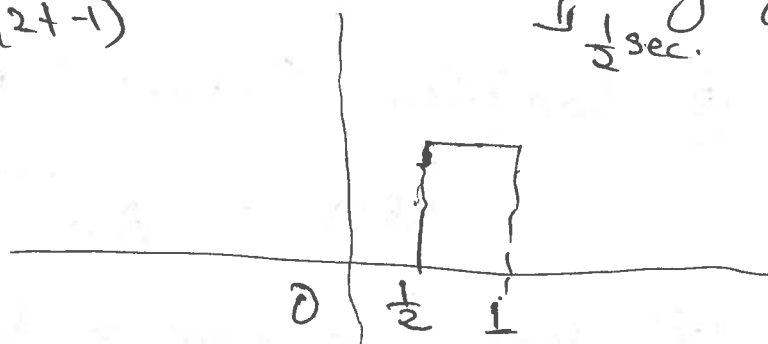

↓ delay by $\frac{1}{2}$ sec.

Linear System -

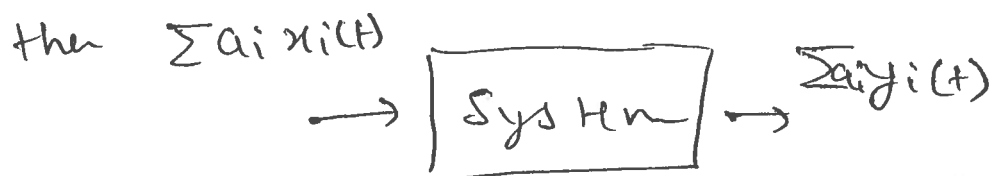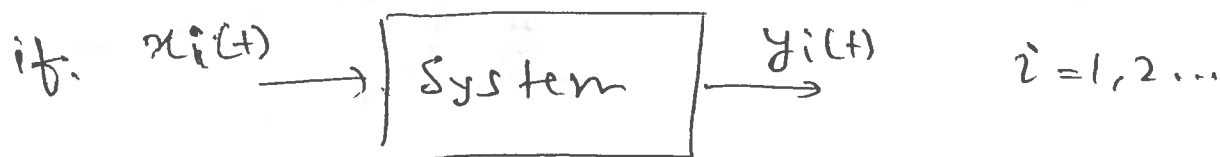

Example: Prove that these system are linear?



a) Amplifier with gain G (trivial)

b) $y(t) = [x(t)]^2$


c) $y(t) = \text{Re} \{ x(t) \}$

Time invariant System

Page-2

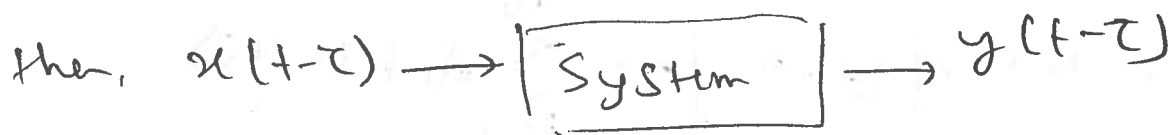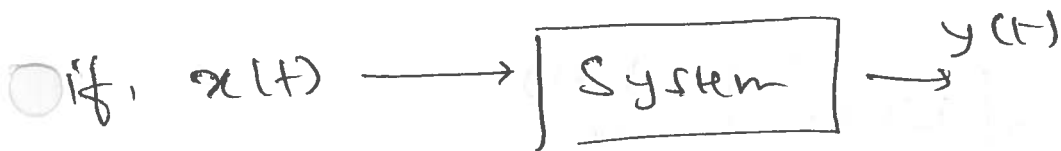

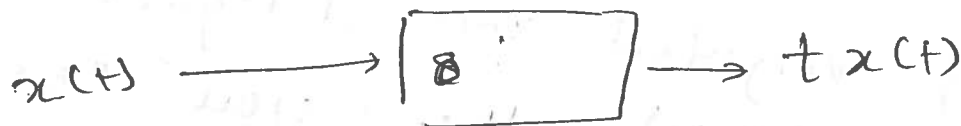
Example: is $y(t) = t x(t)$ a time invariant system?



so, $S(x(t-\tau)) = t x(t-\tau)$


but, $y(t-\tau) = (t-\tau) x(t-\tau) \neq S(x(t-\tau))$

So, not time invariant

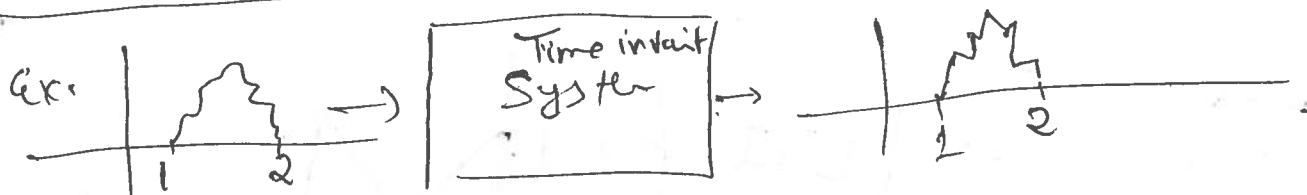

Linear Time invariant System

Example -


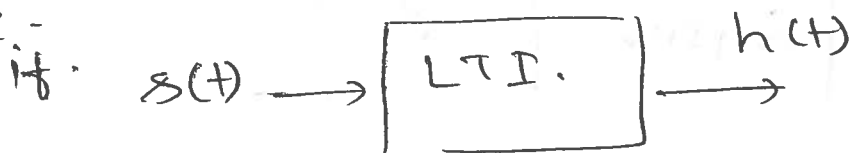


then $\sum_{i=1}^N A_i s(t - \tau_i) \rightarrow \boxed{\text{LTI.}} \rightarrow \sum_{i=1}^N A_i h(t - \tau_i)$

What does this mean?

If you can decompose a ^{Complicated} signal as sum of weighted and delayed basic signal ($s(t)$), then you can easily know the response of the


• LTI System for the complicated signal.

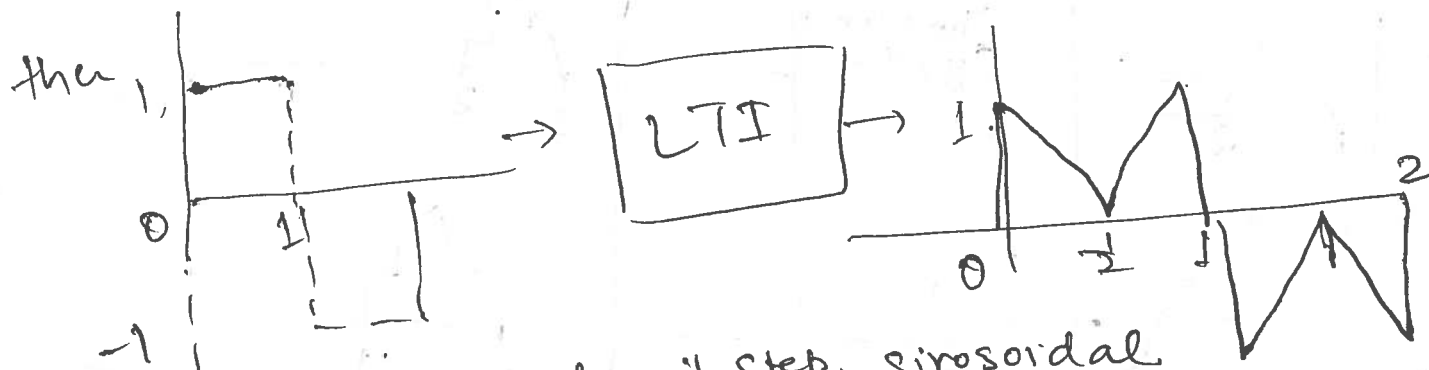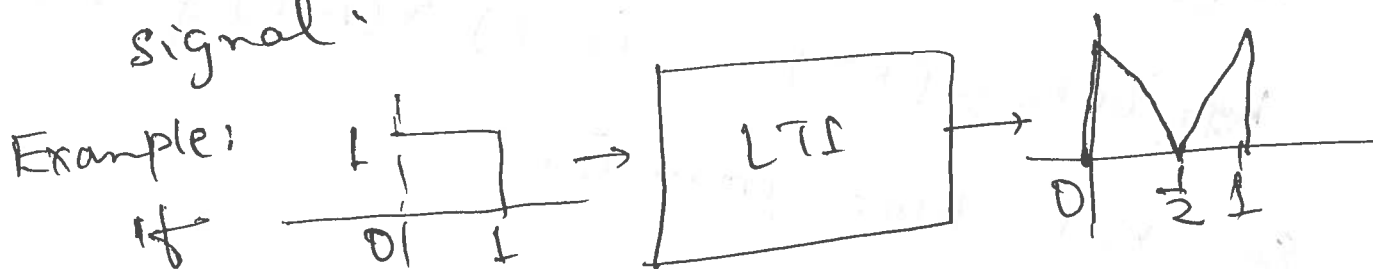

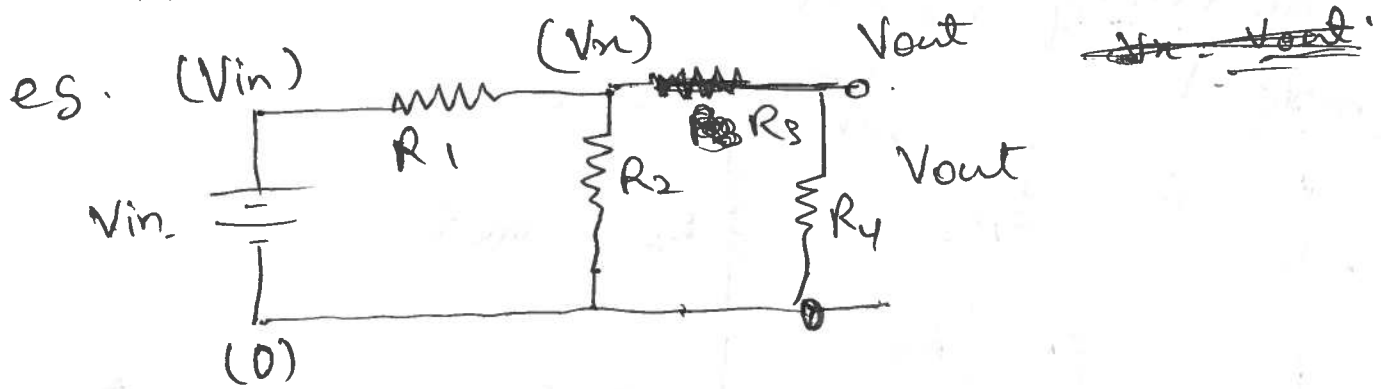
Example - LTI System ad unit step, sinusoidal

Steps to solving a circuit.

- ① Assign voltage to nodes, all known and unknown voltage. Set one voltage as 0V, the choice is arbitrary but generally the negative terminal of voltage source is considered as 0V.



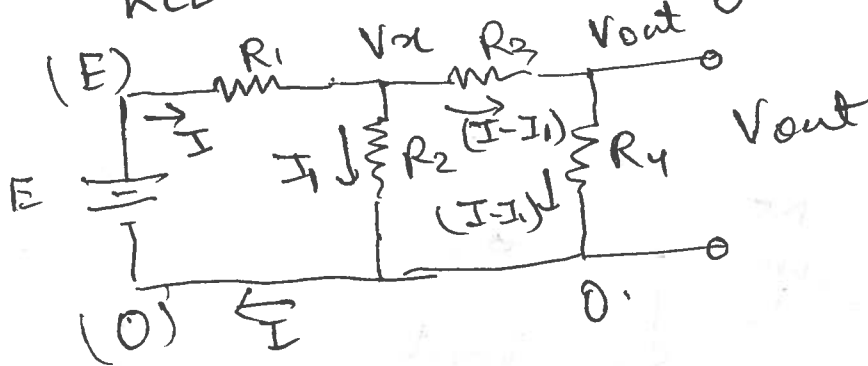- ② Assign current, with direction. Apply KCL while choosing variable names.




~~Check current~~

- ③ Voltage drop in the direction of current flow so, apply KVC and Ohms law with proper sign.
V. drop - ve, V. Rise +ve

- ④ If current flowing through two circuit element is same, they are in series.
 If voltage across two circuit element is same, they are in parallel.
 Simplify circuit as much as possible.


- ⑤ Apply KVL and ohm law to determine all needed parameters.
 (if needed).

Example -1

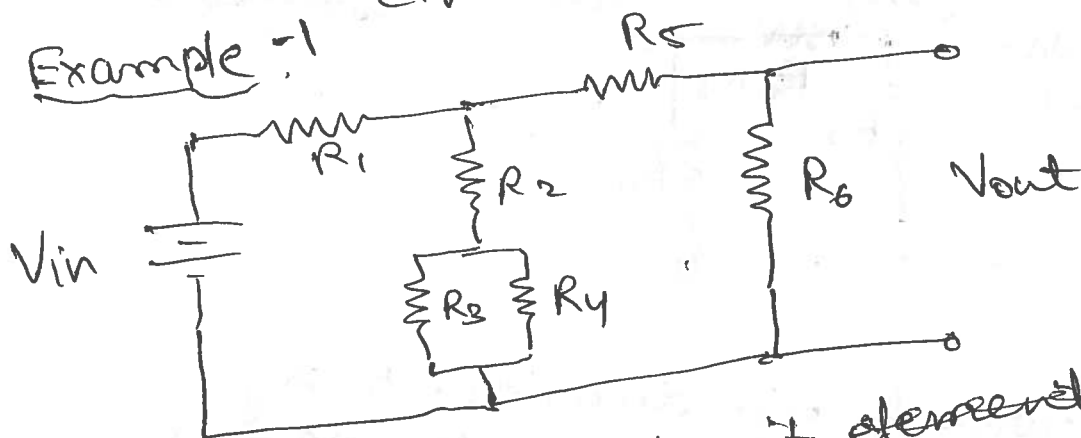

Solve for all circuit elements, current and voltage.

Solution. Step-1 and 2

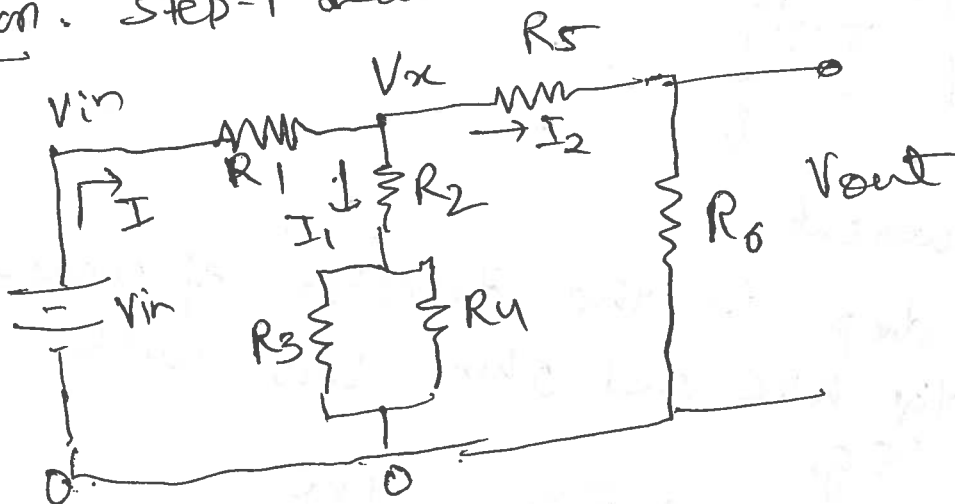

Step-3, 4

Page - 4

$$V_x = V_{in} - IR_1$$

$$I = \frac{V_{in}}{R_1 + (R_2 + R_3 \parallel R_4) \parallel (R_5 + R_6)} \rightarrow \text{Req} \quad \text{--- (1)}$$


$$\text{So, } V_x = \frac{V_{in} \left[(R_2 + R_3 \parallel R_4) \parallel (R_5 + R_6) \right]}{R_{eq}} \quad \text{--- (2)}$$

$$I_1 = \frac{V_x}{R_2 + R_3 \parallel R_4}, \quad I_2 = \frac{V_x}{R_5 + R_6} \rightarrow \text{(2)}$$

$$I_1 + I_2 = I \text{ (check)}$$


$$V_{out} = R_6 \times I_2 = \frac{R_6 V_x}{R_5 + R_6} \text{ (Voltage divider)} \quad \text{--- (4)}$$

Example-2

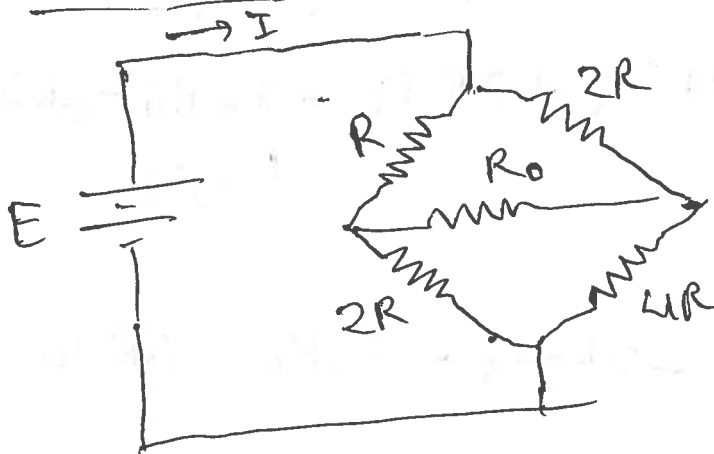

find I ,


Step 1 and 2

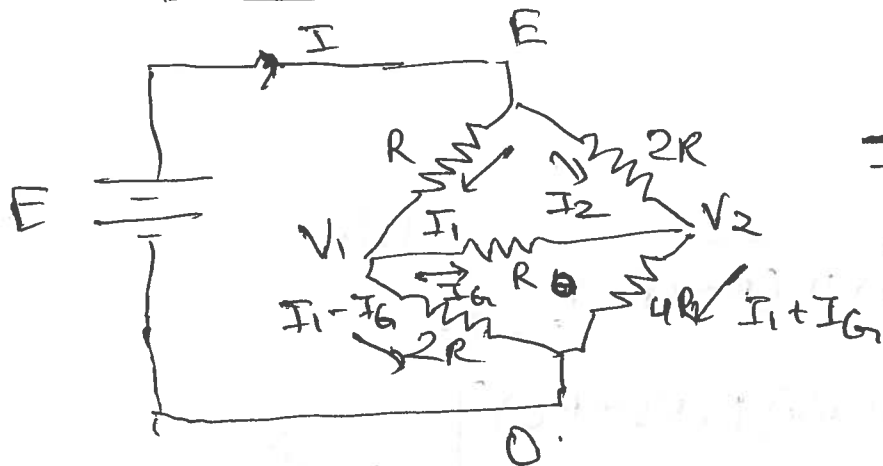

$$I_1 + I_2 = I$$

Step. 3 & 4 \rightarrow So series or parallel

Step. 5. Apply KVL

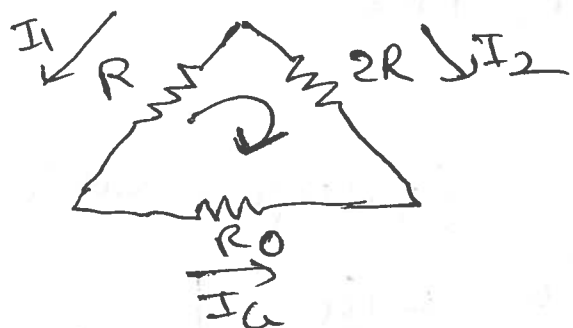

$$-2I_2R + R_0I_6 + I_1R = 0$$

(drop) (rise) (rise)

\rightarrow (1)



$$-I_6R_0 - 4R(I_2 + I_6) + 2R(I_1 - I_6) = 0$$

(drop) (drop) (rise)

\rightarrow (2)

$$\text{eq 2} \Rightarrow -4RI_2 + 2RI_1 - I_6R_0 - 6RI_6 = 0$$

\rightarrow (2)

$\hookrightarrow 2 \times \text{eq (1)} + \text{eq (2)}$

$$\hookrightarrow 0 + 0 - 2R_0I_6 - I_6R_0 - 6RI_6 = 0$$

$$\Rightarrow I_6 = 0$$

As, $I_6 = 0$, we can effectively remove R_0 .

Thus, $I = \frac{E}{3R \parallel 6R} = \frac{E}{2R}$ Ans.