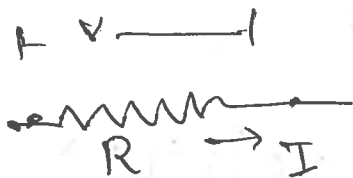


# A. Power Dissipation in resistive circuit


The total power consumed/created by a circuit ~~depends on~~ equals the sum of each elements power.

$$P = \sum_K V_k i_k$$

by convention, positive value of ' $V_k i_k$ ' means consumption of power, and negative value means generation of power.



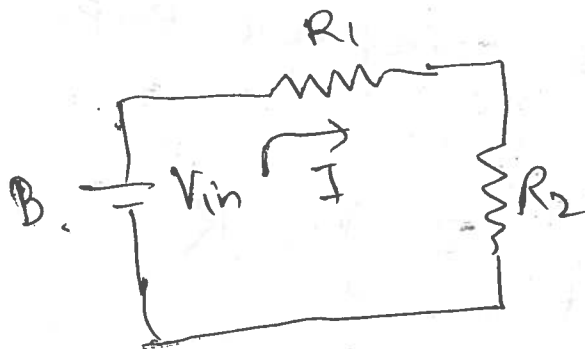Power consumption =  $\frac{V^2}{R} = I^2 R$   
across resistor (always +ve)



$$I = \frac{V_{in}}{R_1 + R_2}$$

$$P_{R_1} = + \frac{V_{in}^2 R_1}{(R_1 + R_2)^2}$$


$$P_{R_2} = \frac{V_{in}^2 R_2}{(R_1 + R_2)^2}$$

$$P_B = (-) V_{in} I_{in}$$

Thus,  $P_B + P_{R_1} + P_{R_2} = 0$

$$= (-) \frac{V_{in}^2}{R_1 + R_2} = -P_{R_1}$$

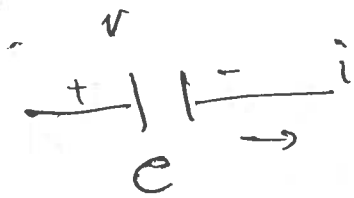
## B. Circuits with Capacitors and inductors



$$\dot{i} = C \frac{dv}{dt}$$



$$V = L \frac{di}{dt}$$

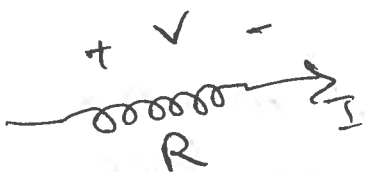


$$V = IR$$

Let us assume that the ~~voltage~~ all the sources in the circuit are complex exponentials.

$$V_{in}(t) = V_{in} e^{j2\pi f t}$$

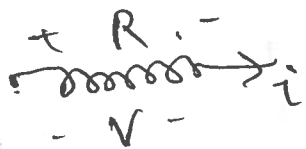
this implies that all the voltages and current are also complex exponentials.



$$V = V e^{j2\pi f t}$$

$$i = \left(\frac{V}{R}\right) e^{j2\pi f t}$$

$$Z = \frac{V}{I} = R$$

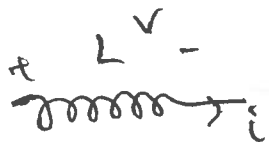


$$\text{if } i(t) = I e^{j2\pi f t}$$

$$\text{then, } v(t) = LI(2j\pi f) e^{j2\pi f t}$$

$$v(t) = L(2\pi f j) i(t)$$

$$Z = \frac{v(t)}{i(t)} = L(2\pi f)j$$

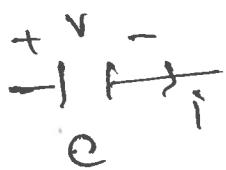

if  $v(t) = V e^{j2\pi f t}$

$$i(t) = C V (2\pi f j) e^{j2\pi f t}$$

$$Z = \frac{V(t)}{i(t)} = \frac{1}{2\pi f C j}$$

$$= C(2\pi f j) v(t)$$

~~Thus, V-I relationship for all circuit element~~


Thus, major consequence of assuming complex exponential voltage and currents is that the ratio  $z = \frac{V}{I}$  for each element does not depend on time, but does depend on source frequency.

All circuit laws (KCL, KVL) applies under this formulation.


Steps to solve circuits having RLC.

- ① Even if it's not, pretend the source is a complex exponential
- ② Solve circuit using the impedance method - (series, parallel, KCL, KVL etc) in frequency domain.
- ③ Get the output for the actual input.

Example.

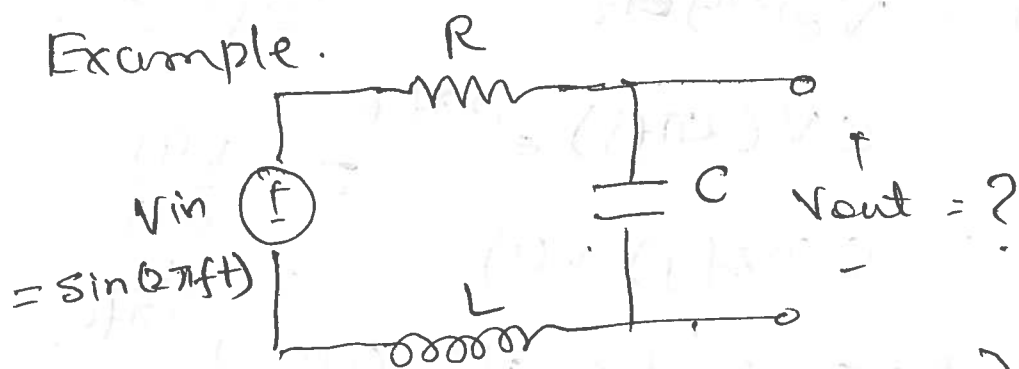

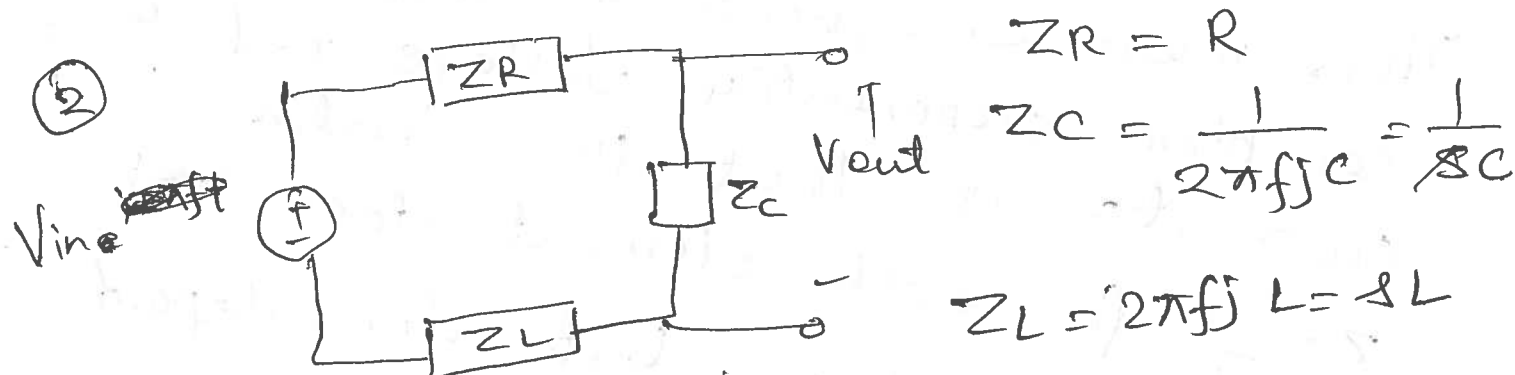①  $V_{in} = V_{in} e^{j2\pi ft}$  (assume)



$$V_{out} = \frac{Z_C}{Z_R + Z_L + Z_C} V_{in}$$

$$= \left[ \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} \right] V_{in}$$

$$V_{out} = \frac{V_{in}}{RCs + LCs^2 + L} ; s = 2\pi f j$$

$$V_{out} = \frac{V_{in}}{RC(2\pi f j) - LC(4\pi^2 f^2) + L}$$

$$= \frac{V_{in}}{(1 - 4\pi^2 f^2 LC) + j2\pi R C f} \quad (\text{Cartesian})$$

$$V_{out} = \frac{V_{in}}{\sqrt{[1 - 4\pi^2 f^2 LC]^2 + (2\pi R C f)^2}} e^{j\left[ \frac{2\pi f R C}{4\pi^2 f^2 LC - 1} \right]} \quad (\text{polar})$$

③  ~~$V_{in} = \text{Im}[V_{in}]$~~   
~~(actual)~~  $\downarrow$  ~~assumed~~

$$V_{out} = V_{out} e^{j2\pi f t}$$

$$= \frac{V_{in}}{\sqrt{(-)^2 + (-)^2}} e^{j\theta} e^{j2\pi f t}$$

$$V_{in} = \sin(2\pi f t) = \text{Im}[e^{j2\pi f t}]$$

③

$$V_{out} = \frac{1}{\sqrt{(-)^2 + (-)^2}} \sin(2\pi f t + \theta)$$

# Power in frequency domain

$$V(t) = |V| e^{j\omega t}$$

$$P_{av} = \frac{1}{2} \operatorname{Re}(VI^*)$$

$V, I \rightarrow$

Complex  
amplitude

$$= \frac{1}{2} \operatorname{Re}(2) |I|^2$$

$$= \frac{1}{2} \operatorname{Re}\left(\frac{1}{Z}\right) |V|^2$$

- 1) Only Real part of impedance contribute to long term power dissipation
- 2) Only the resistor dissipate power.
- 3) L, C dissipate no power in long term.
- 4) these statement apply only for sinusoidal sources.

Transfer function

$$\frac{V_{out}}{V_{in}} = H(f)$$


$$= |H(f)| \angle(H(f))$$

↑  
magnitude

→ phase.

Implicit is that input and output are complex exponentials, and  $V_{in}, V_{out}$  are the complex amplitude.


Example

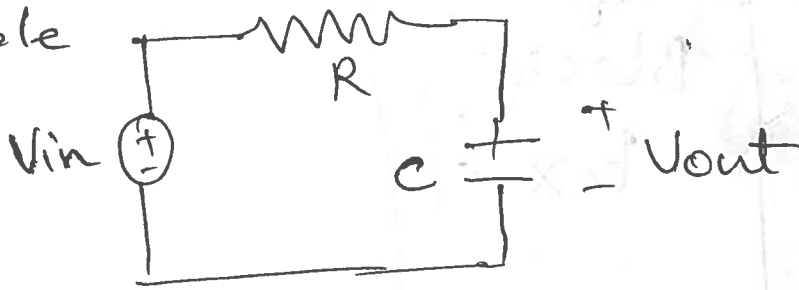

$$H(f) = \frac{1}{j2\pi fRC + 1}$$


$$|H(f)| = \frac{1}{\sqrt{1 + 4\pi^2 f^2 R^2 C^2}}$$
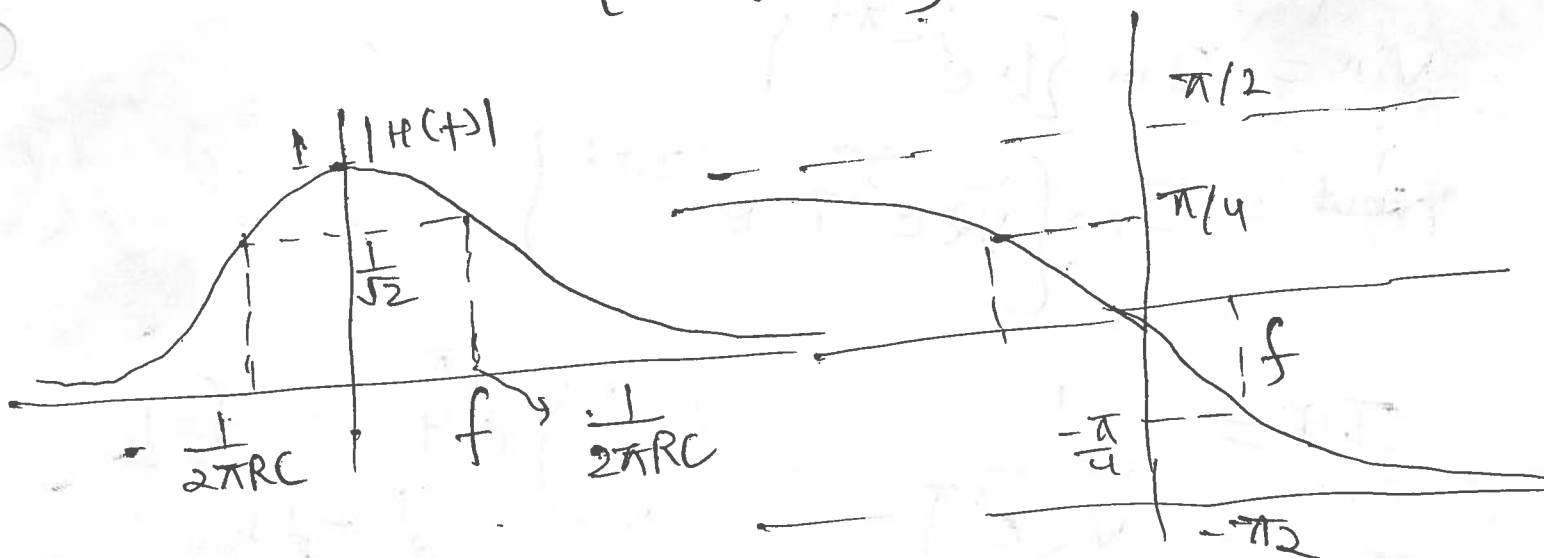
$$\angle H(f) = \tan^{-1} \left[ \frac{-2\pi fRC}{1} \right]$$



- Note -
- 1)  $|H(-f)| = |H(f)|$
  - 2)  $\angle H(-f) = -\angle H(f)$
  - 3) cutoff frequency =  $\frac{1}{2\pi RC}$

Ex. 1

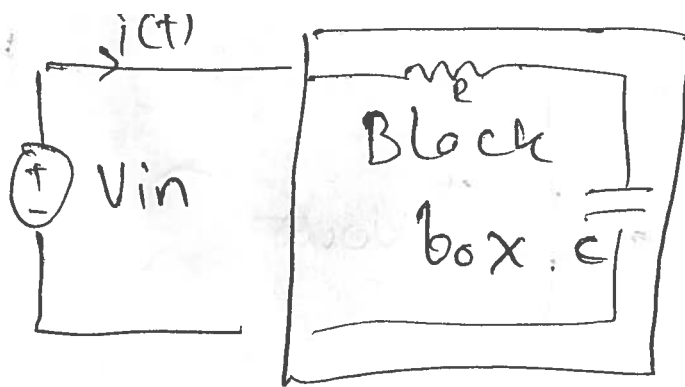


a)  $V_{in}(t) = \sin(2\pi f t)$   
 $i(t) = \sqrt{2} \cos(2\pi f t - \frac{\pi}{4})$   
 $\because \sin(\frac{\pi}{2} + \theta) = \cos(\theta)$   
 $= \sqrt{2} \sin(2\pi f t + \frac{\pi}{4})$

$$V_{in} = \text{Im} \{ 1 \cdot e^{j2\pi f t} \}$$

$$i_{out} = \text{Im} \left\{ \sqrt{2} e^{j\frac{\pi}{4}} e^{j2\pi f t} \right\}$$

$$T.F. = \frac{1}{\sqrt{2} e^{j\frac{\pi}{4}}} = \left( \frac{1}{\sqrt{2}} \right) e^{-j\frac{\pi}{4}} \quad f = L$$
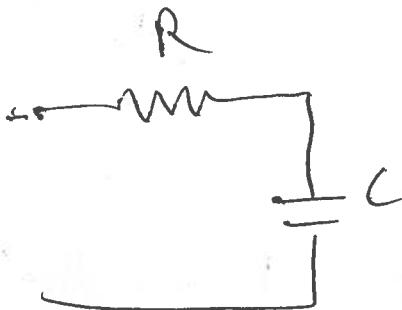
$$= \frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}$$



$$T.F. = \frac{R}{R + \frac{1}{2\pi j f C}}$$

So,  $R = \frac{1}{2}$ ,  $\frac{1}{2} = \frac{1}{2\pi f C}$   
 $\Rightarrow C = \frac{1}{\pi}$